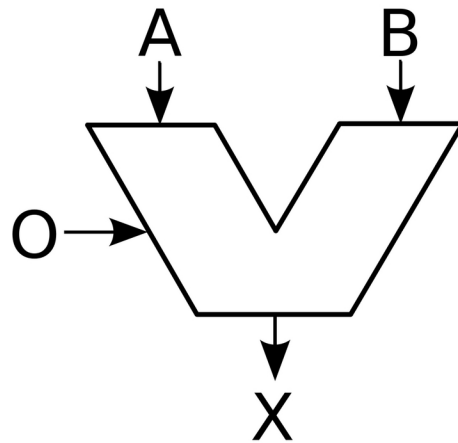


# ALU3000

## What is ALU3000?

-ALU3000 (Arithmetic Logic Unit 3000) is a well designed modern combinational digital electronic that performs arithmetic and logic operations. Construction of ALU3000 is shown below.



ALU (image 1.1)

## -What components does ALU3000 have?

ALU3000 is a combinational circuit which consists of PIPO registers, arithmetic unit, logic unit and multiplexer.

## What operations can ALU perform?

- It depends on how ALU is designed. ALU3000 can perform 4 Arithmetic and 4 Logic operations which are shown in table.

Operation list table(table 1.1)

Sel	Operation	Type
000	$A + B$	Arithmetic Unit
001	$A - B$	
010	$A + 1$	
011	$\max(A,B)$	
100	$A \text{ AND } B$	Logic Unit
101	$A \text{ OR } B$	
110	NOT A	
111	$A \text{ XOR } B$	


*\*Magnitude comparison part will be examined in page 6.*

# D-LATCH


What is D-Latch?

- D-Latch is electronic circuit that can be used to store 1 bit data.

RTL

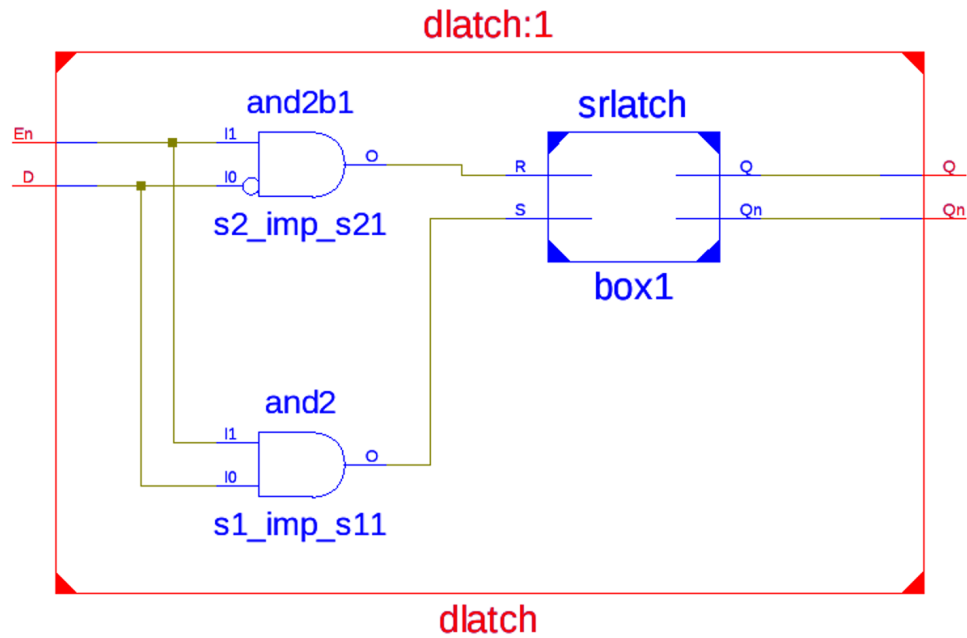

## Test Bench Result

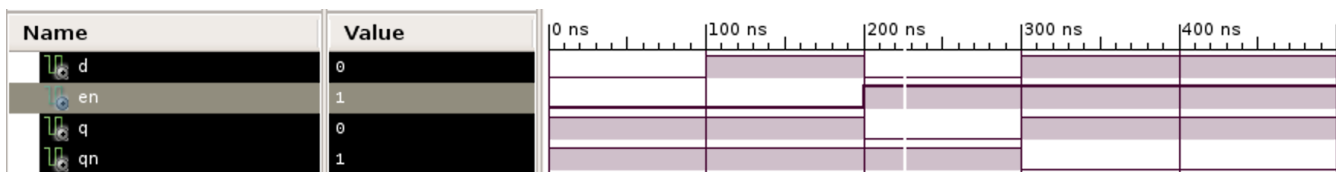


D	En	Q	Qn
0	0	X	X
1	0	X	X
0	1	0	0
1	1	1	0

*D-Latch truth table (table2.1)*

# PIPO REGISTER

PIPO Register ( Parallel Input Parallel Output Register) is data storage device that perform data loading in parallel mode.

## RTL

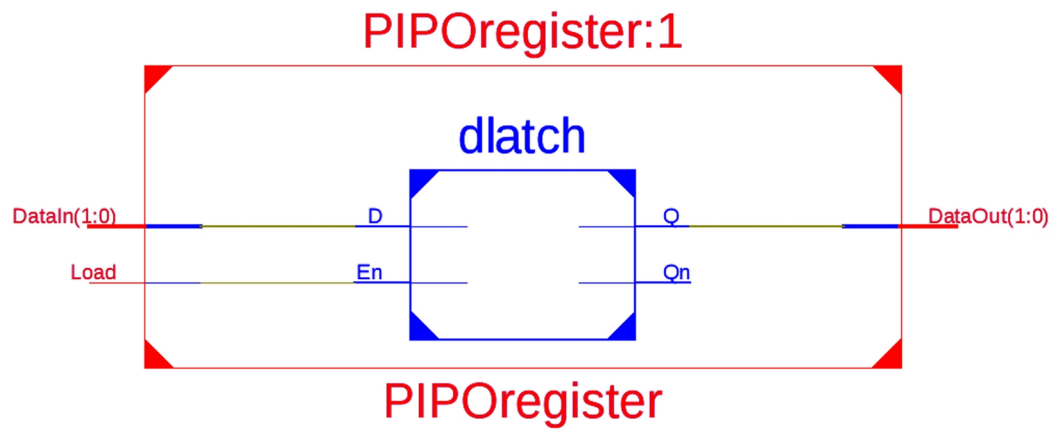

## Test Bench Graph




- Pipo register loads when load bit is '1'.


# ARITHMETIC UNIT

Arithmetic Unit consists of 3 binary adder subtractor, a 4 to 1 Mux and a magnitude comparator.

## RTL

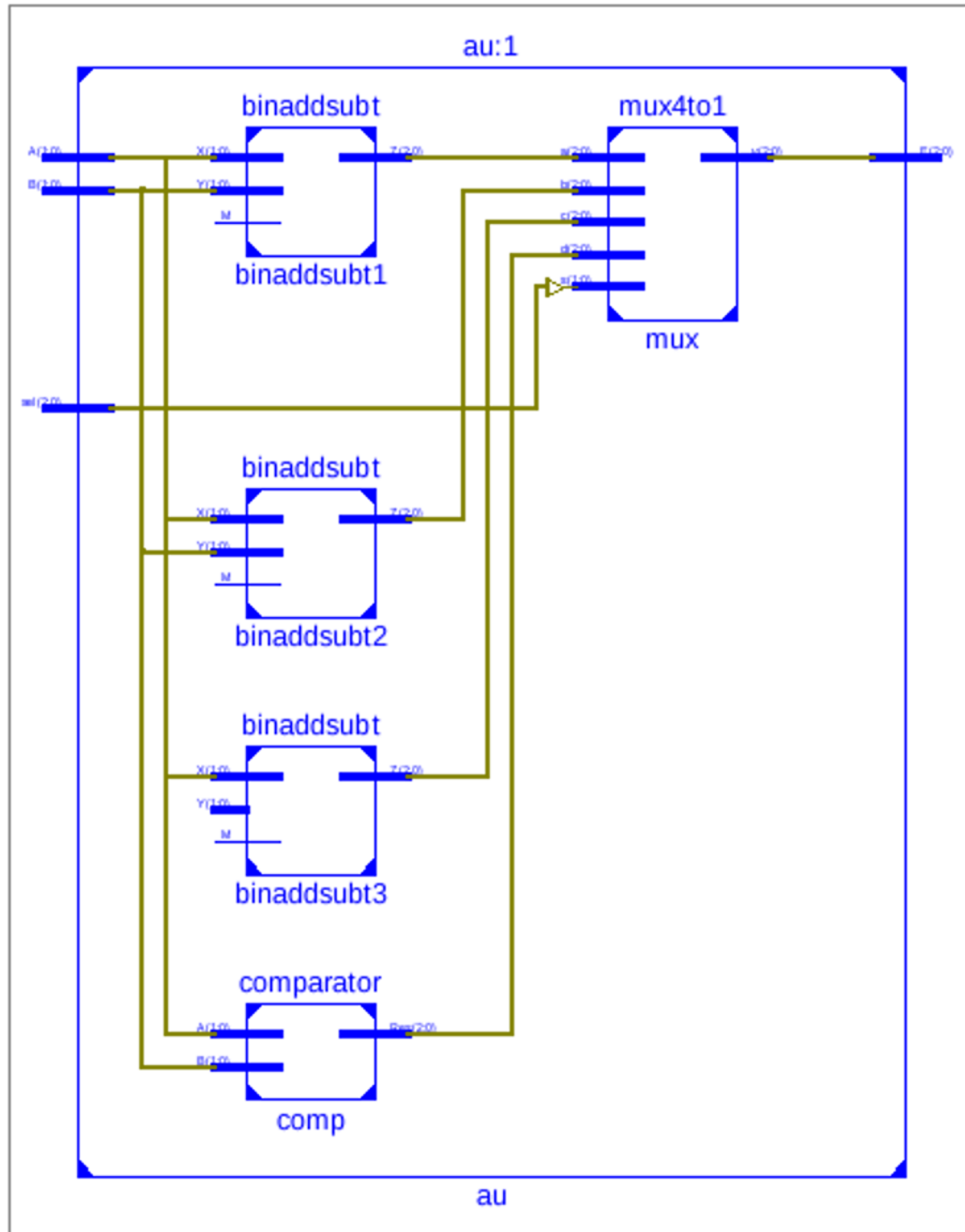


## Binary Adder Subtractor

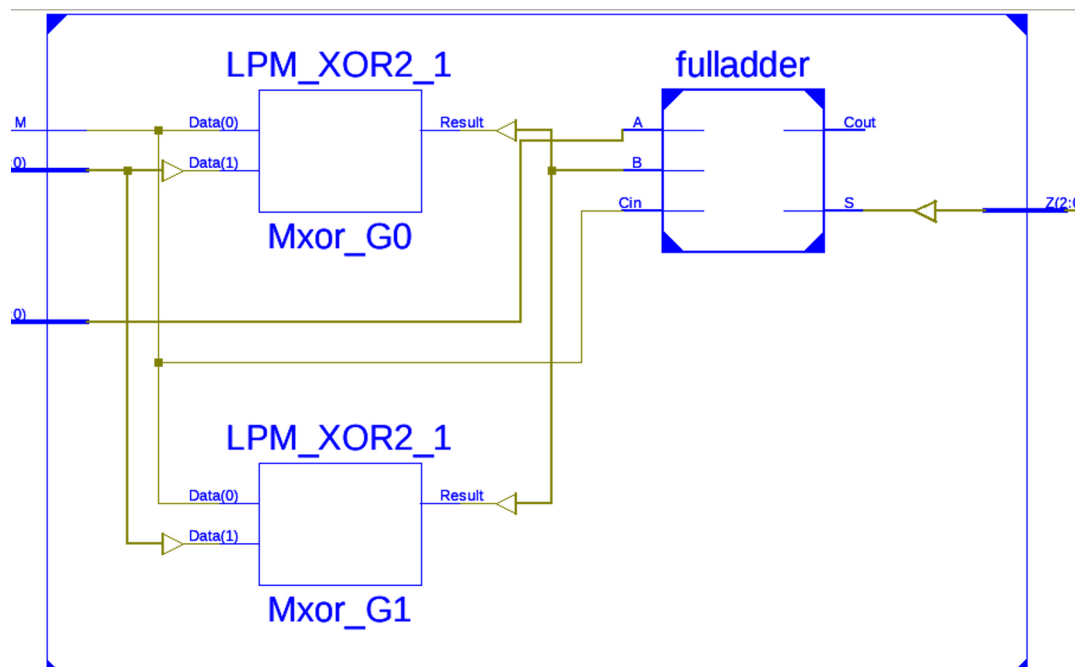

- Binary adder subtractor gets 3 input and give 1 output.
- 2 inputs for data and 1 input for selection bit.
- Selection bit allows adder subtractor to perform allow/subtract operation.

## Magnitude Comparator

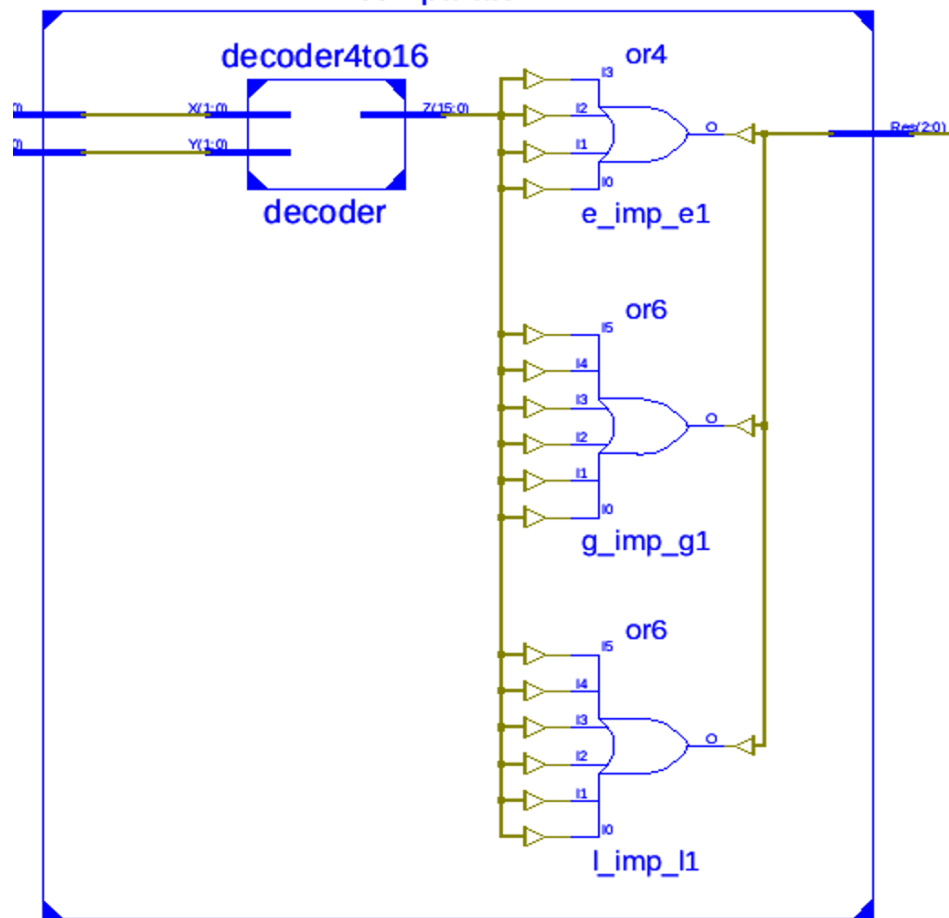


- Magnitude comparator gets 2 inputs and gives 1 output.
- The size of the output is 3 and it is in order of “GEL”
- Which means;
  - $A > B \Rightarrow \text{“100”}$
  - $A = B \Rightarrow \text{“010”}$
  - $A < B \Rightarrow \text{“001”}$

## Test Bench Result

		A+B	A-B	A+1	max(A,B)
a[1:0]	11				
b[1:0]	01				
sel[2:0]	001	000	001	010	011
f[2:0]	110	100	110		100
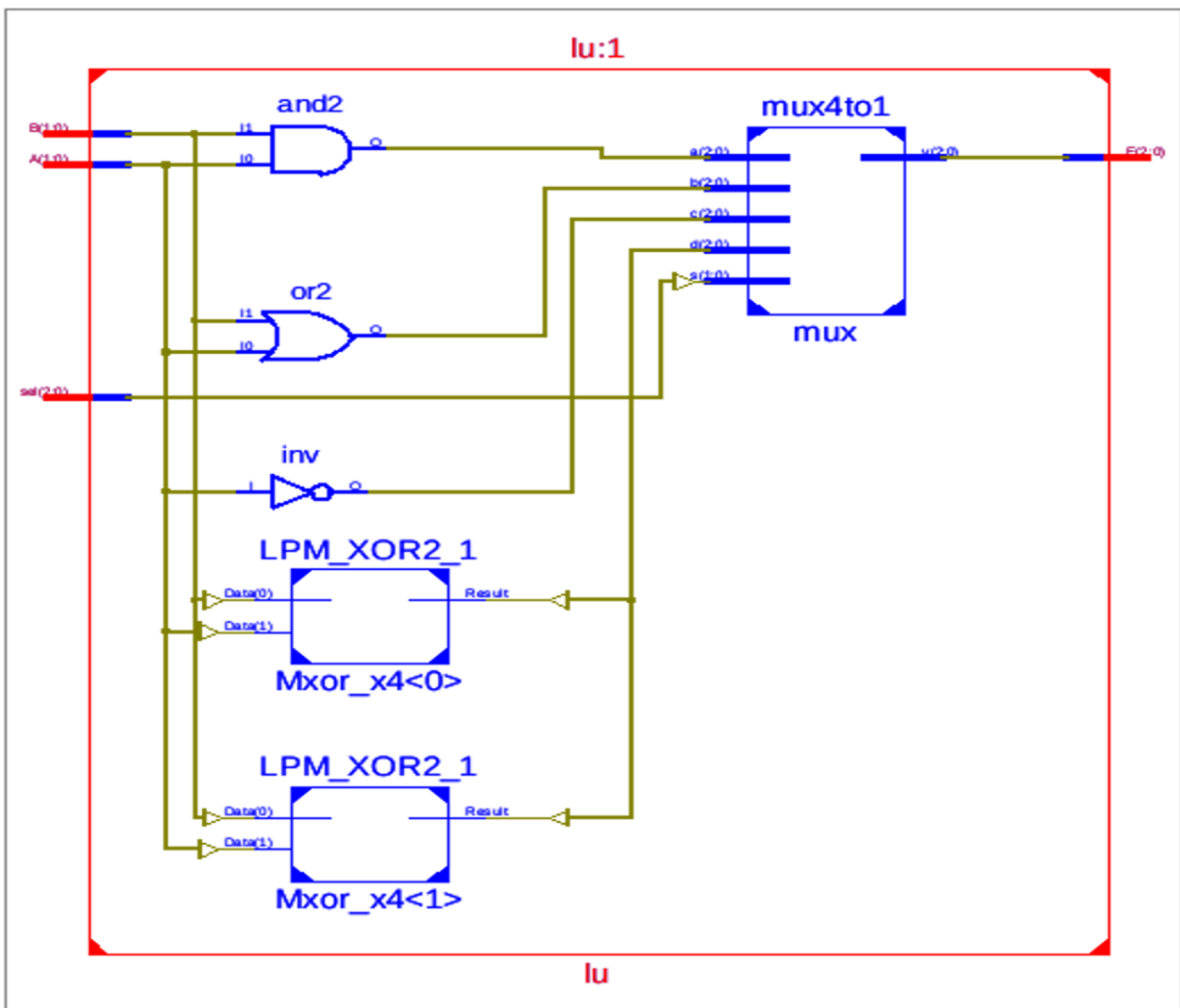
## LOGIC UNIT

Logic Unit is the unit which process logic functions, such as AND, OR, XOR, NOT, RTL




## Test Bench Result

		AND	OR	NOT A	XOR
a[1:0]	01				
b[1:0]	10				
sel[2:0]	100	100	101	110	111
f[2:0]	000	000	011	010	011

## 4x1 MUX

-4x1 mux allows us to choose which operation to perform in logical unit and arithmetic unit by Sel(1:0) “last 2 bit of Selection signal”

## RTL

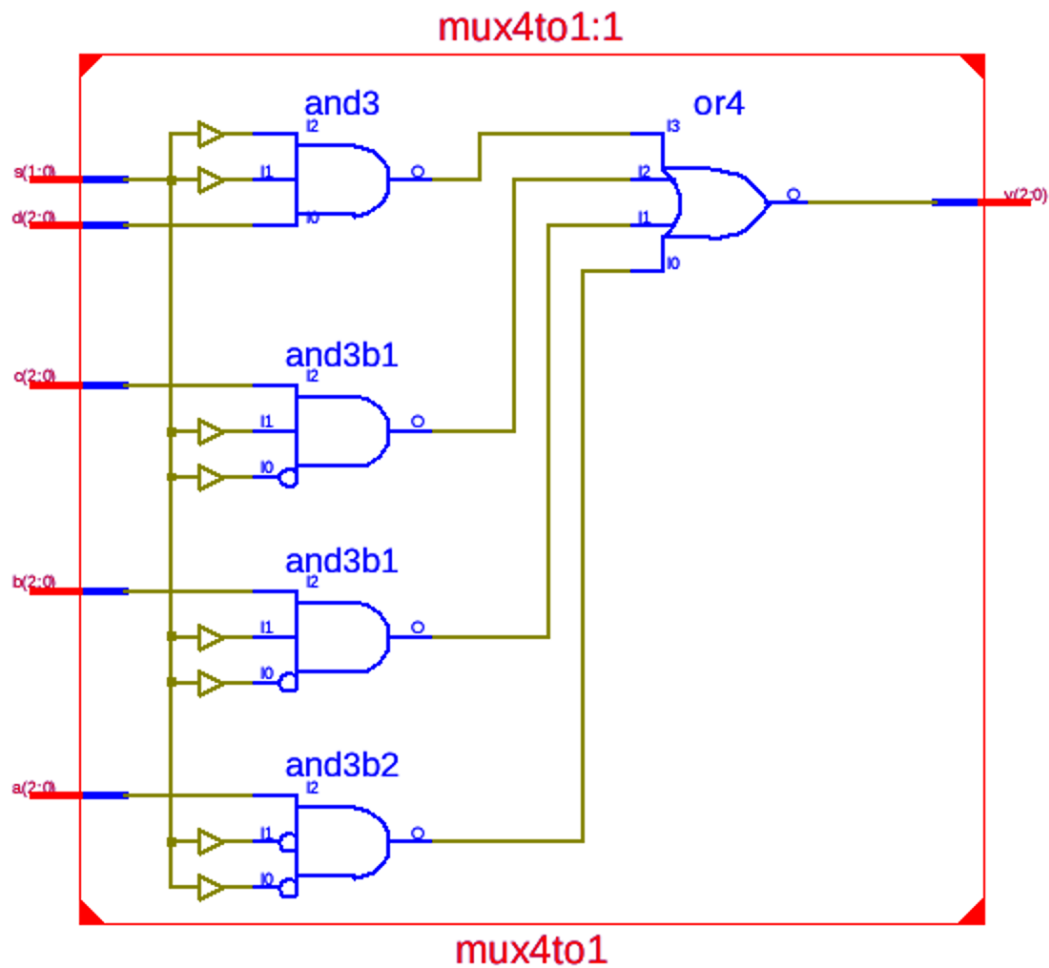




## MUX (2 TO 1)

This MUX takes the output of Arithmetic Unit and Logic Unit as input and msb of 'sel' as a selection bit. If msb of 'sel' is 1 it gives to corresponded output of Logic Unit, else it gives Arithmetic Unit's output.

### RTL

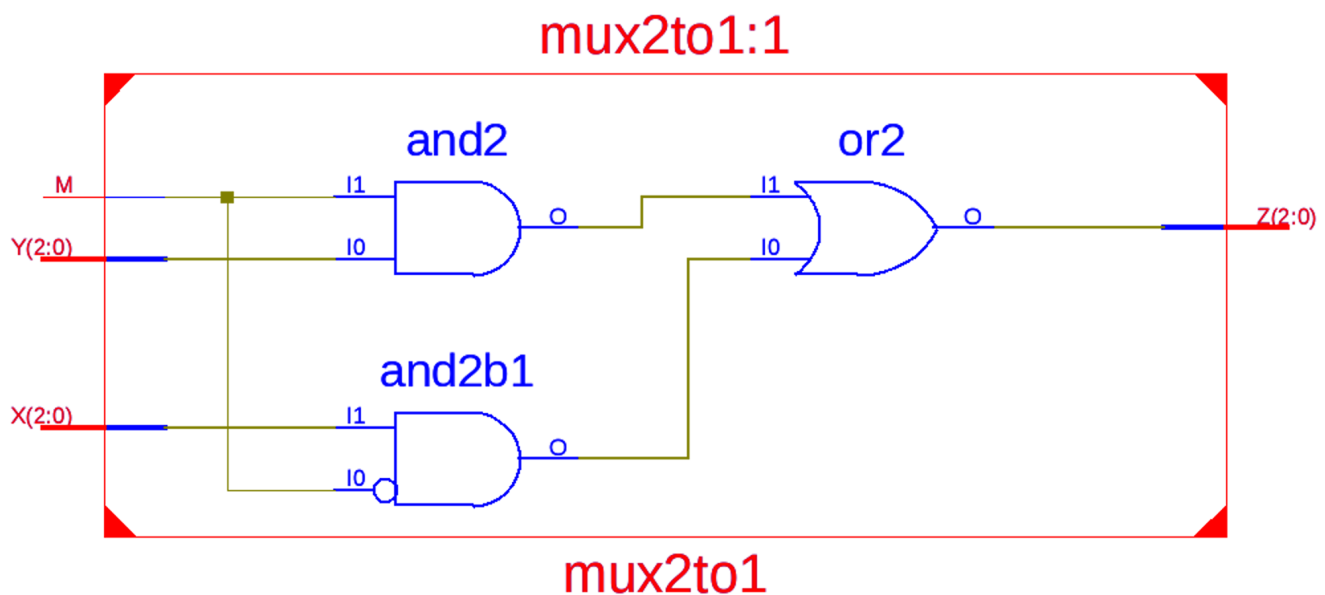

-2x1 multiplexer gets 3 inputs. M is *msb* of selection signal, X is output of arithmetic unit and Y is output of logic unit.

-It allows us to choose whether perform arithmetic or logic operation by the msb of selection input.


### Test Bench Result

x[2:0]	010	001
y[2:0]	101	110
m	0	
z[2:0]	010	001 110

\*msb = Most significant bit

## ALU

### Rt1

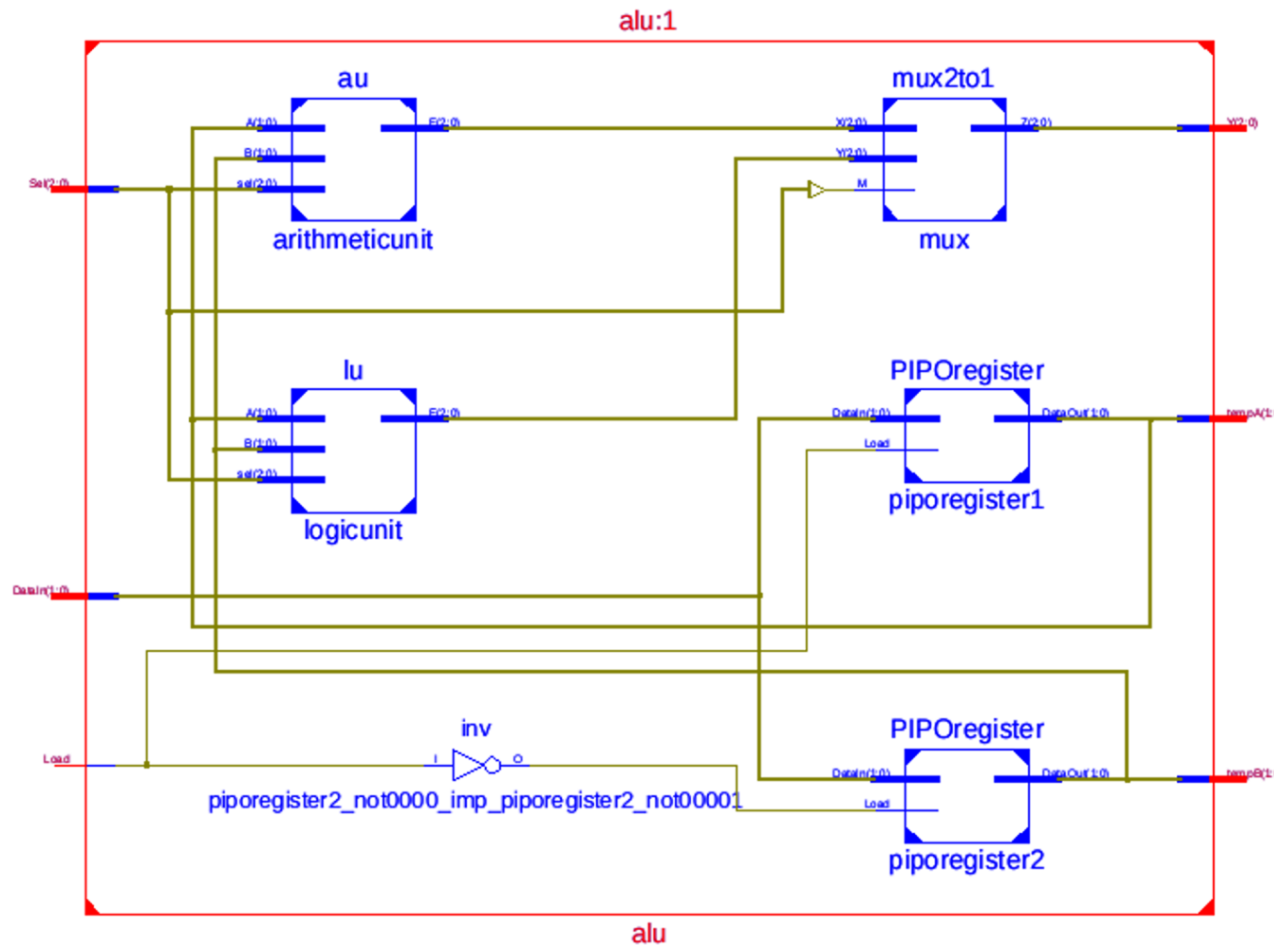

-This is the top module of project.

## Test Bench Result

datain[1:0]	00	10	01
load	1		
sel[2:0]	000	000	000
tempa[1:0]	00	10	01
tempb[1:0]	11		
y[2:0]	011	101	010

\*We can see that it follows the order of table 1.1

## Summary

- ALU is logical components which perform logical and arithmetical operations.
- ALU may consists of different components and it varies by the design of it.
- For ALU3000, magnitude comparator, binary adder subtractor, sr-latch, d-latch, PIPO register etc. used.

## Further Improvements

- To improve to ALU 3000 there are three steps that I can take
  - 1- Expanding the operation list
    - Shifting, rotating etc. can be add
  - 2- Optimizing the system
    - For me, only way to that is decreasing the total transistor amount.

## External Links

- <https://www.youtube.com/watch?v=mOVOS9AjgFs> \*youtube video by Ben Eater about ALU
- <https://www.allaboutcircuits.com/projects/how-to-build-your-own-discrete-4-bit-alu/> similar project by Robin Mitchell. August 18,2016.
- <https://www.allaboutcircuits.com/projects/how-to-build-your-own-discrete-4-bit-alu/> useful resource by Gojko Babic

## **Source Code can be found in**

<https://github.com/itsjustaplant/ALU3000> (by me of course)